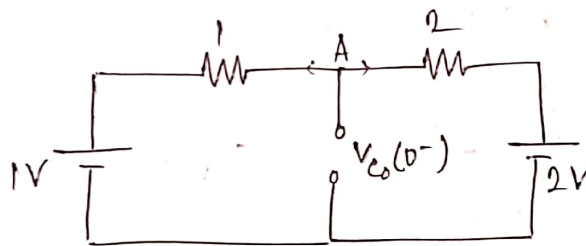


When the switch is shifted from the position of P to Q, we will consider as $t = 0$.

from that point of view,

the equivalent ckt ~~is~~ at $t = 0^-$ (At $t = 0^-$



the ckt will be in steady state so, capacitor will act as open ckt)

From the

$$V_{Co}(0^-) = \frac{4}{3} V.$$

$$\therefore V_{Co}(0^+) = \frac{4}{3} V.$$

As $t = 0^+$, abrupt change of voltage is not possible.

Using KCL at node A,

$$\frac{V_{Co}(0^-) - 1}{1} + \frac{V_{Co}(0^-) - 2}{2} = 0$$


$$\therefore V_{Co}(0^-) - 1 + \frac{V_{Co}(0^-) - 2}{2} = 0$$

$$\therefore \frac{3}{2} V_{Co}(0^-) = 2$$

$$\therefore V_{Co}(0^-) = \frac{4}{3} V.$$


The equivalent ckt at $t=0^+$

2

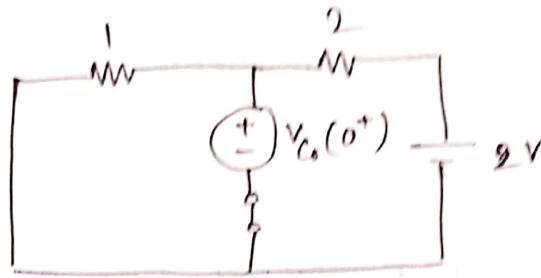

At $t=0^+$, the capacitor will act as short ckt.

2. The s-domain equivalent ckt is -

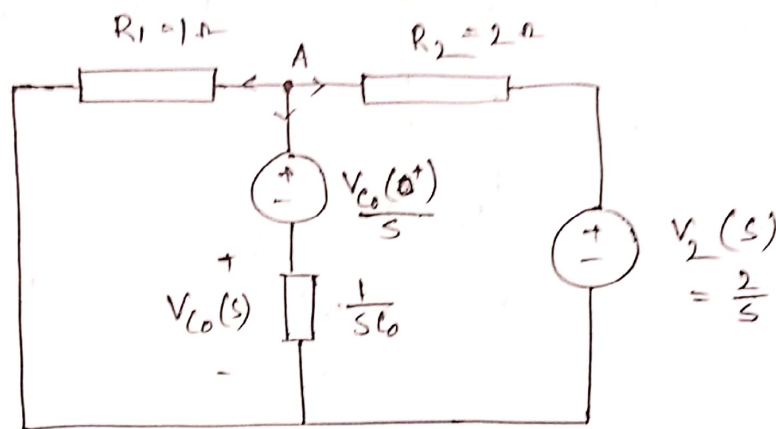

$$C_0 = 1 \mu F$$

$$V_C(0^+) = \frac{4}{3}$$

$$\frac{V_A - 0}{1} + \frac{V_A - \frac{4}{3s}}{1/sC_0} + \frac{V_A - 2/s}{2} = 0$$

3. Applying KCL at node A,

$$\frac{V_C(s) - 0}{1} + \frac{V_C(s) - V_C(0^+)}{1/sC_0} + \frac{V_C(s) - V_2(s)}{2} = 0$$

$$\therefore V_C(s) \left(\frac{3 + 2sC_0}{2} \right) = \frac{3 + 4Cs}{3s}$$

$$V_{C_0}(s) = \frac{2(3 + 4s^2)}{3s(3 + 2s)} = \frac{6 + 8s^2}{3s(3 + 2s)}$$

$$V_{C_0}(s) + sC_0 V_{C_0}(s) - sC_0 V_{C_0}(0^+) + \frac{V_{C_0}(s)}{2} - \frac{V_2(s)}{2} = 0$$

$$\frac{3}{2} V_{C_0}(s) + sC_0 V_{C_0}(s) - sC_0 \times \frac{4}{3s} - \frac{1}{s} = 0$$

$$\left[\text{As } V_{C_0}(0^+) = \frac{4}{3s} \right]$$

$$\left(\frac{3}{2} + sC_0 \right) V_{C_0}(s) = \frac{1}{s} + \frac{4C_0}{3} = \frac{3 + 4sC_0}{3s}$$

$$V_{C_0}(s) = \frac{2(3 + 4sC_0)}{3s(3 + 2sC_0)} = \frac{6 + 8sC_0}{3s(3 + 2sC_0)}$$

$$V_{C_0}(s) = \frac{6^2}{3s(3+2C_0s)} + \frac{8C_0}{3(3+2C_0s)} \quad 2$$

$$\begin{array}{c} A \\ \leftarrow \quad \rightarrow \\ \hline 3 \end{array}$$

$$= \frac{2}{2C_0s\left(s + \frac{3}{2C_0}\right)} + \frac{8C_0}{9 + 6C_0s}$$

$$= \frac{A}{s} + \frac{B}{s + \frac{3}{2C_0}} + \frac{4}{3\left(s + \frac{3}{2C_0}\right)}$$

$$= \frac{2/3}{s} - \frac{2/3}{s + \frac{3}{2C_0}}$$

$$+ \frac{4}{3} \cdot \frac{1}{\left(s + \frac{3}{2C_0}\right)}$$

$$A = \frac{1}{C_0 \left(\frac{3}{2C_0}\right)}$$

$$= \frac{2}{3}$$

$$B = \frac{1}{C_0 \times \left(-\frac{3}{2C_0}\right)}$$

$$= -\frac{2}{3}$$

$$4. \quad \therefore V_{C_0}(t) = \frac{2}{3} u(t) - \frac{2}{3} e^{-3/2C_0 t} u(t) + \frac{4}{3} e^{-\frac{3}{2C_0} t} u(t)$$

$$= \frac{2}{3} u(t) + \frac{2}{3} e^{-\frac{3}{2C_0} t} u(t)$$

(3)

$$v_{C_0}(t) = \frac{2}{3} \left(1 + e^{-1.5 \times 10^6 t} \right) u(t)$$

5.

$$\begin{aligned} v_{C_0}(0^-) &= v_{C_0}(0^+) = \lim_{t \rightarrow 0^+} v_{C_0}(t) \\ &= \frac{4}{3} V. \end{aligned}$$

$$\begin{aligned} v_{C_0}(\infty) &= \lim_{t \rightarrow \infty} v_{C_0}(t) \\ &= \frac{2}{3} V. \end{aligned}$$

